

DESIGN OF MITSUBISHI XPANDER OXYGEN SENSOR VOLTAGE SIGNAL SIMULATOR

Student's name: LÊ ANH ĐỨC- 1852327

Instructor: Ph.D. TRẦN ĐĂNG LONG

I. INTRODUCTION

- Project on The Mitsubishi Xpander Oxygen Sensor Voltage Signal .
- The aim of the project is to simulate 2 signals OS1 and OS2 (Oxygen sensor Signal 1 and Oxygen sensor Signal 2).
- The requirement of the project that the output signals closely resembles the oxygen sensor signals of Mitsubishi Xpander.

1. General information

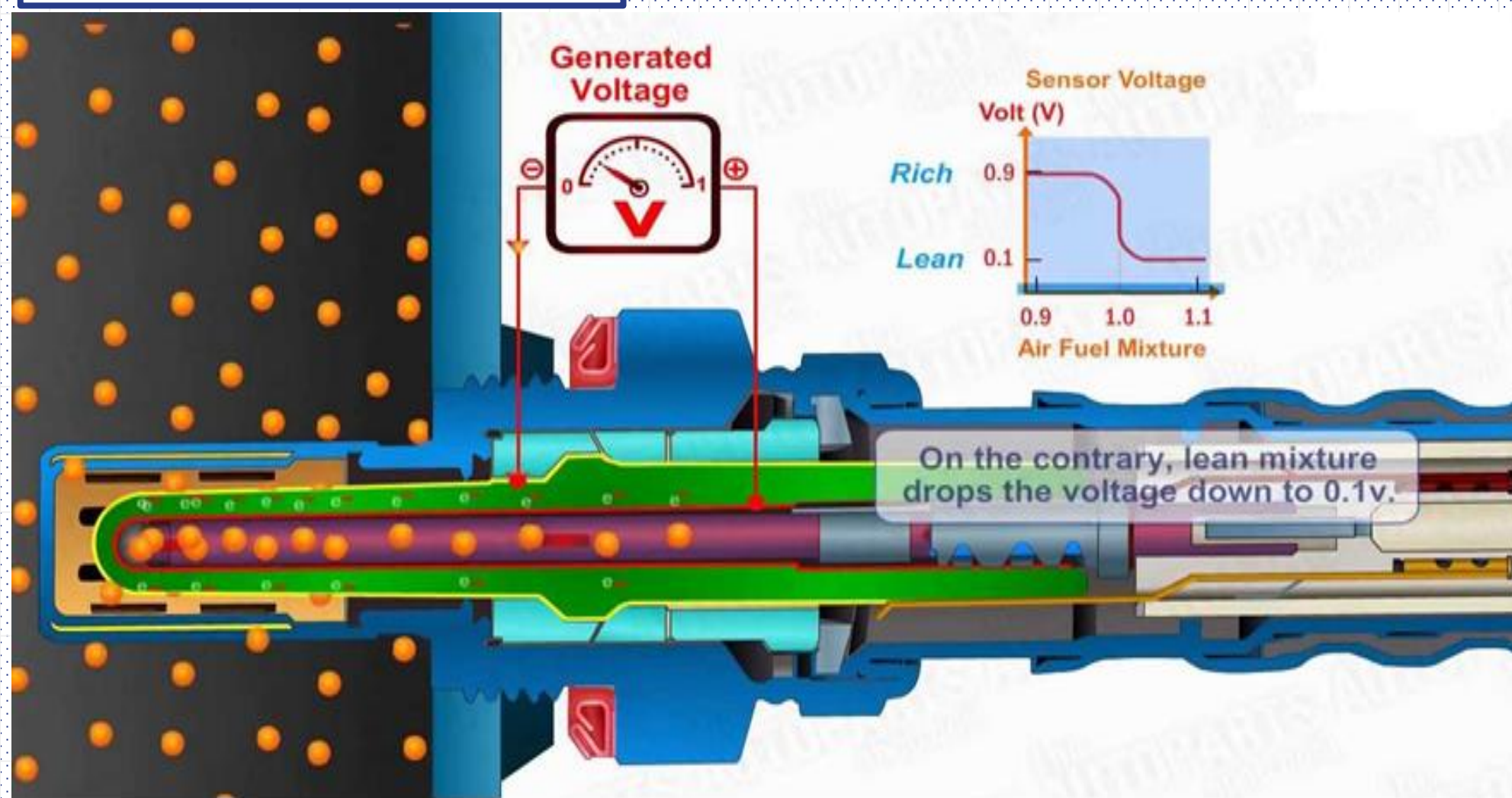


Figure 1.1: Narrow-band oxygen sensor

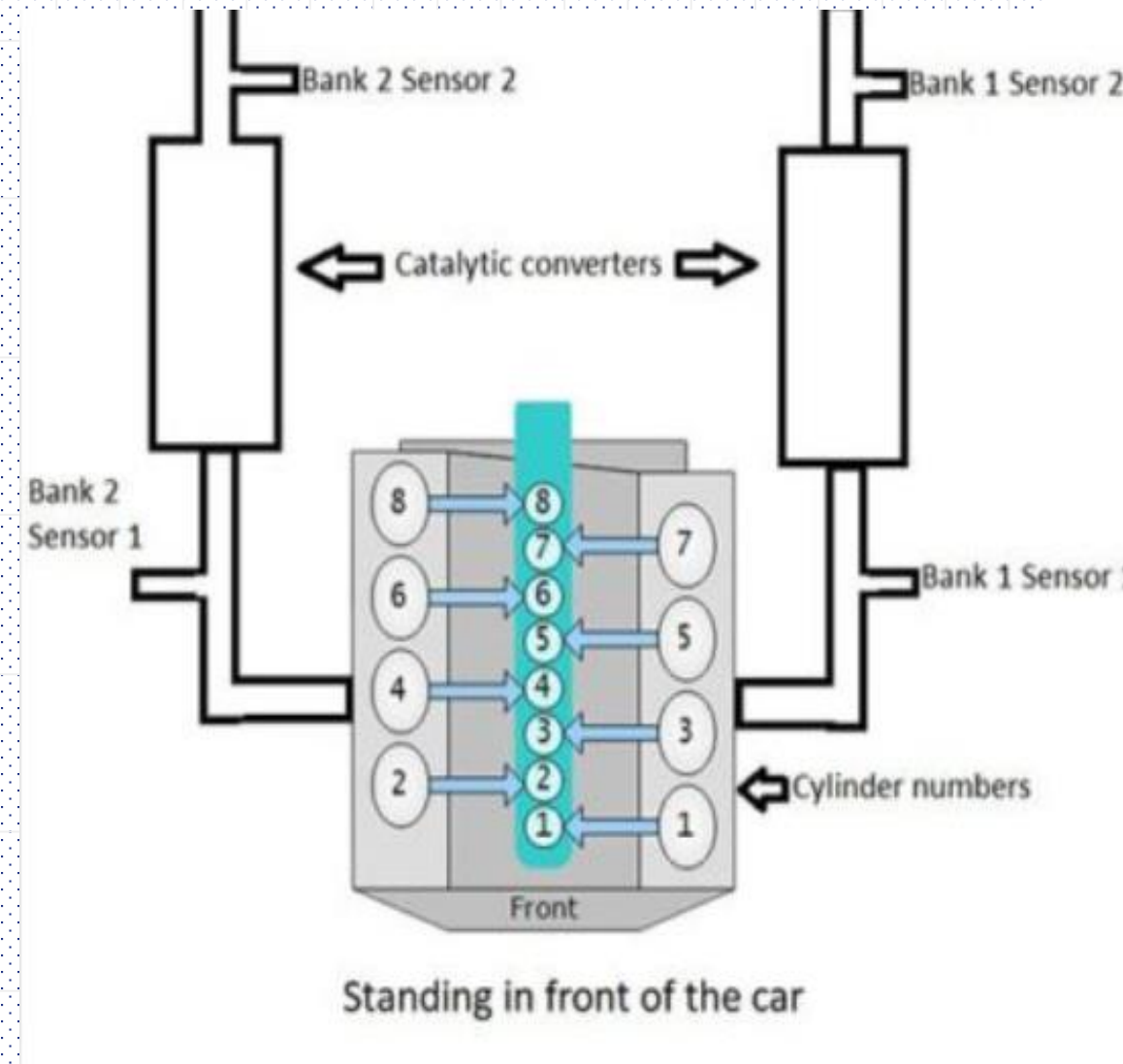


Figure 1.2: Location oxygen sensor

- Located within the emissions control system.
- Ensure that the engine is running at top condition
- The differences in oxygen levels between the bulb and the outside atmosphere generates voltage.

II. GENERAL LAYOUT DESIGN

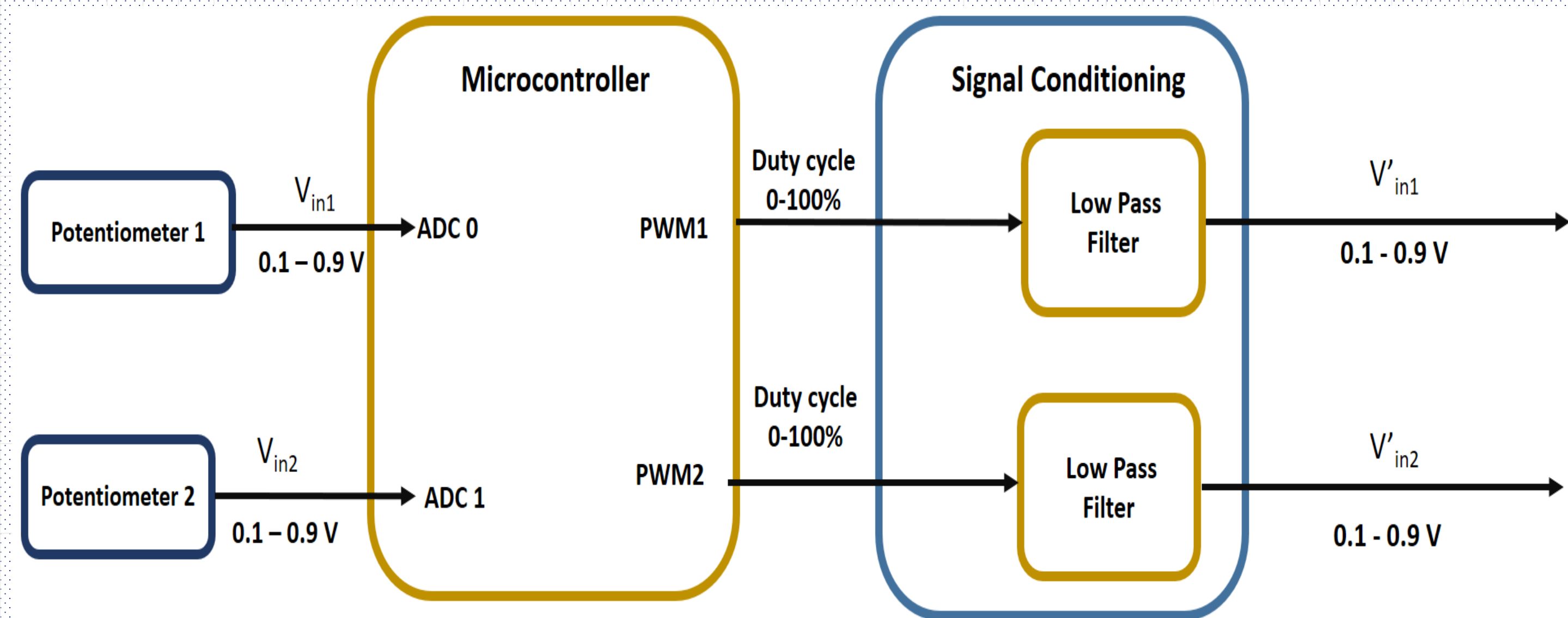


Figure 2.1: Structure diagram of oxygen sensor simulator

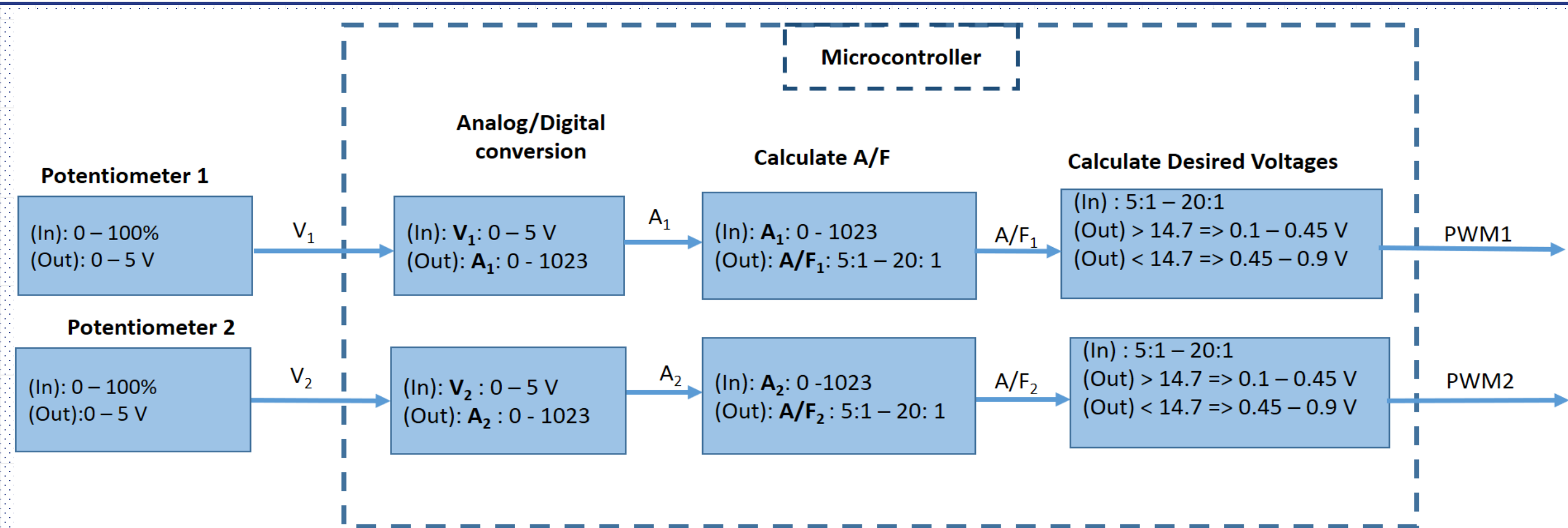


Figure 2.2: Principle diagram of oxygen sensor simulator

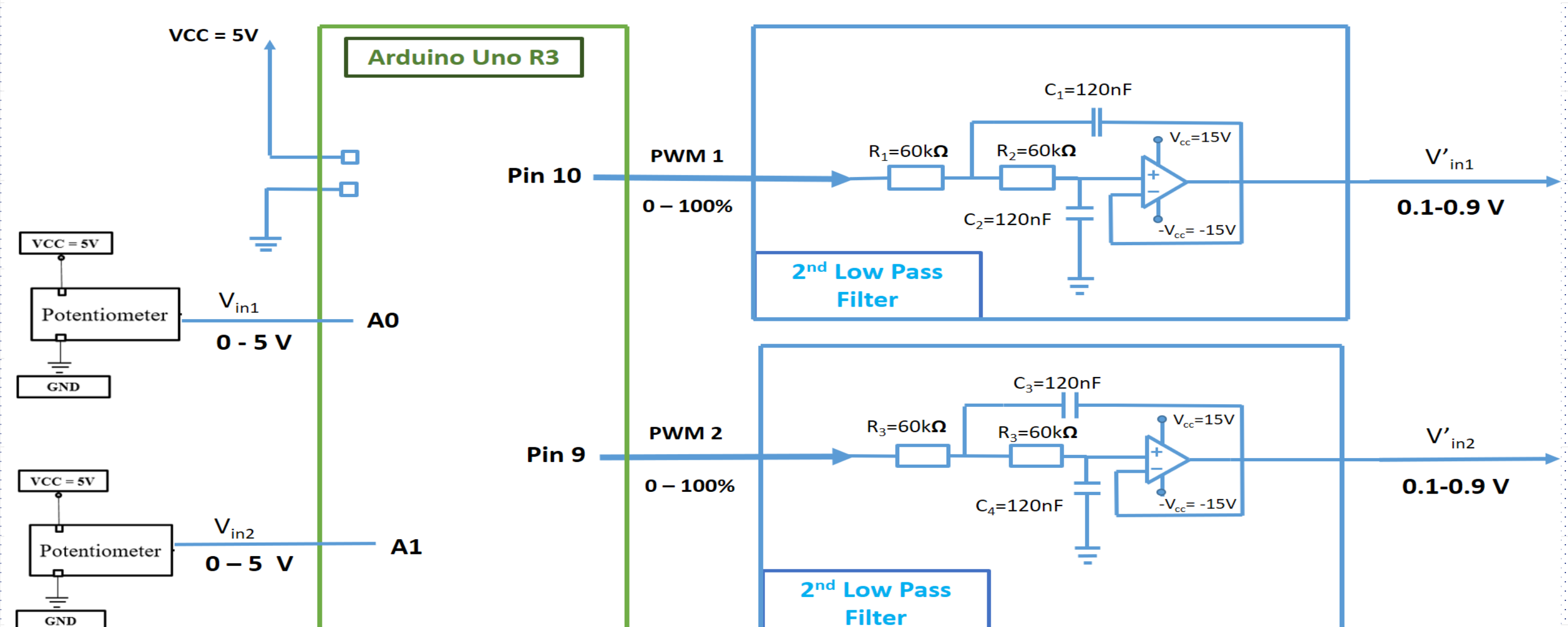


Figure 2.3: Electrical scheme

III. TECHNICAL DESIGN

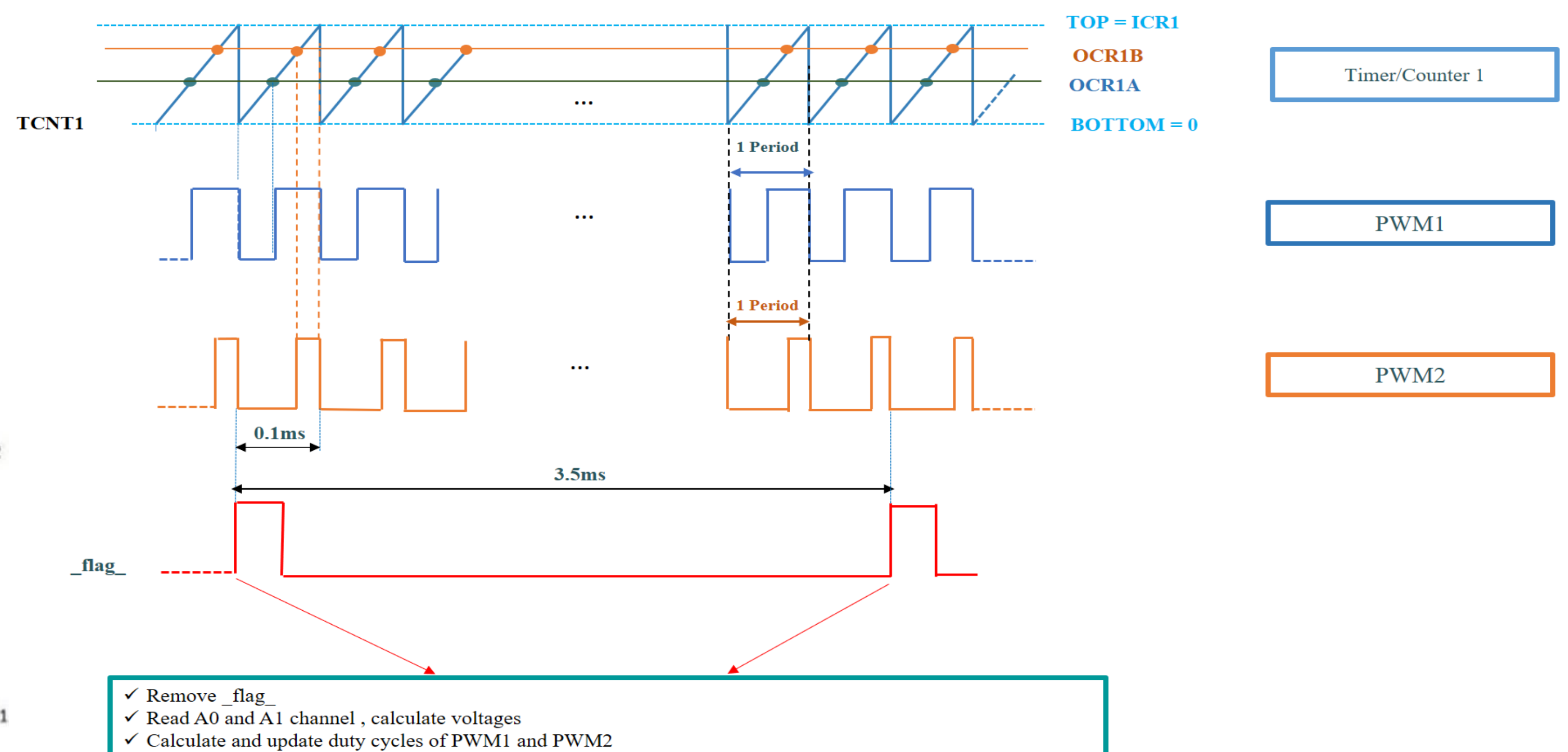


Figure 3.1: Timing diagram of the program

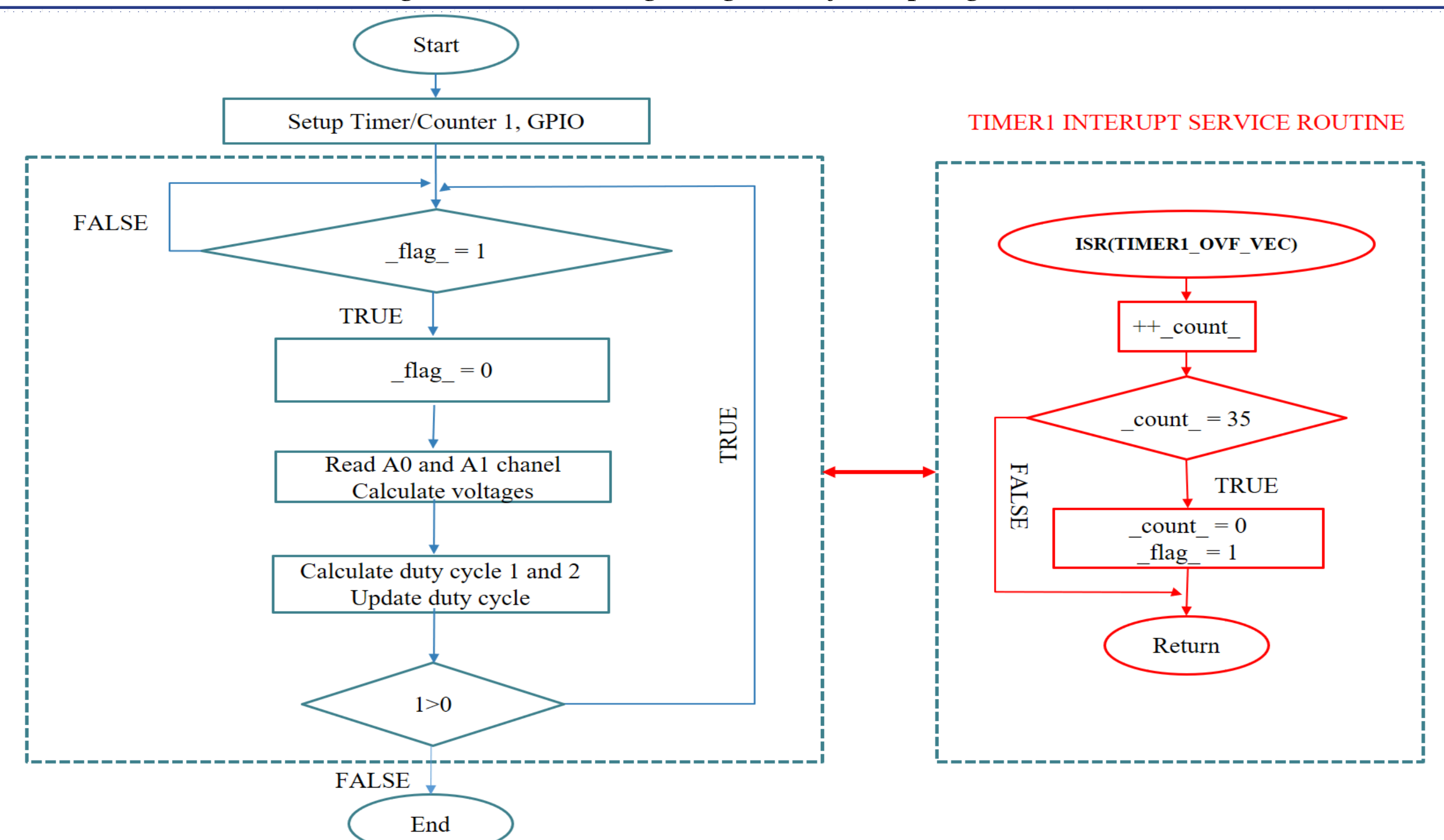


Figure 3.2: Algorithms diagram of the program

IV. SIMULATION AND RESULTS

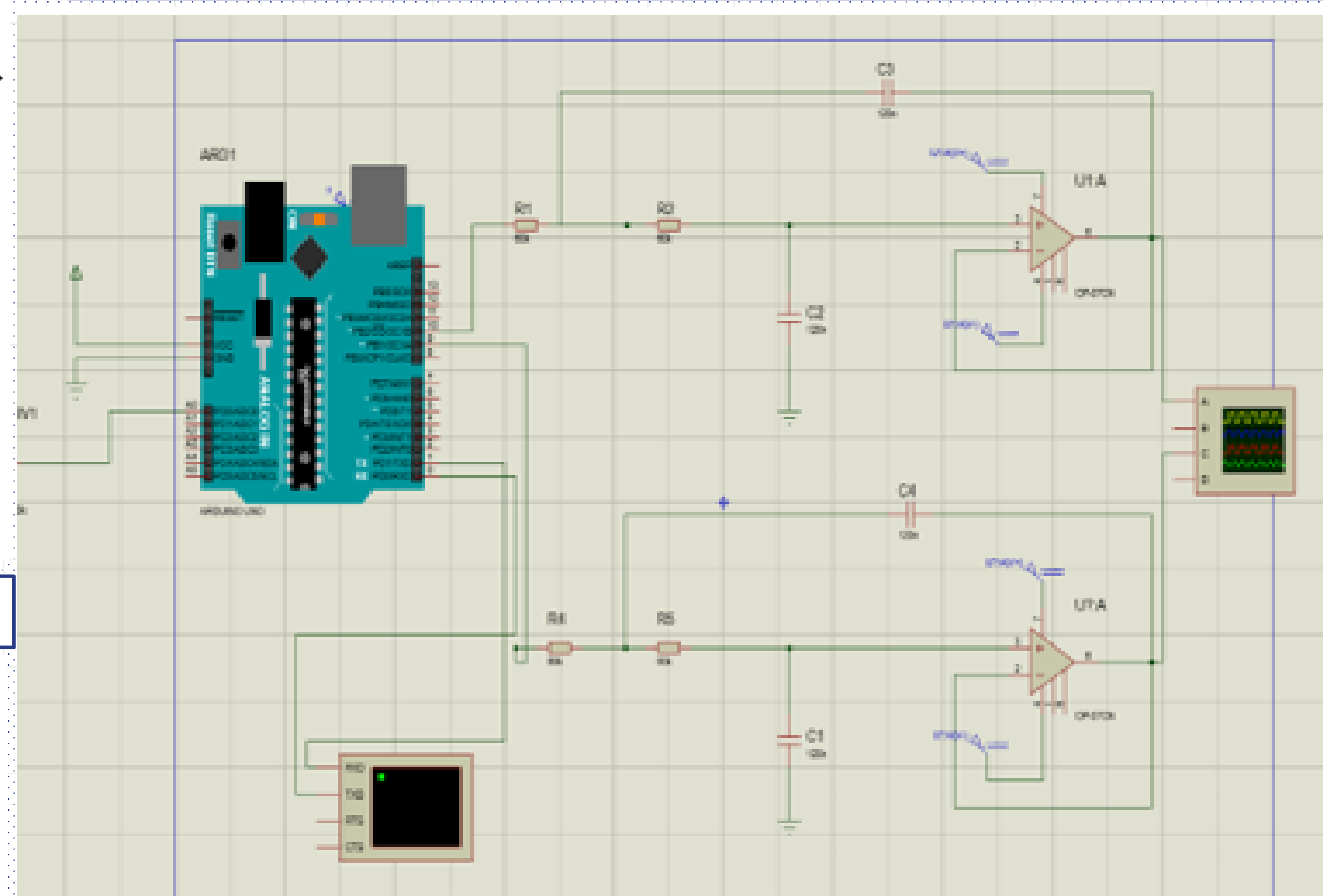


Figure 4.1: Electrical diagram in Proteus Simulation

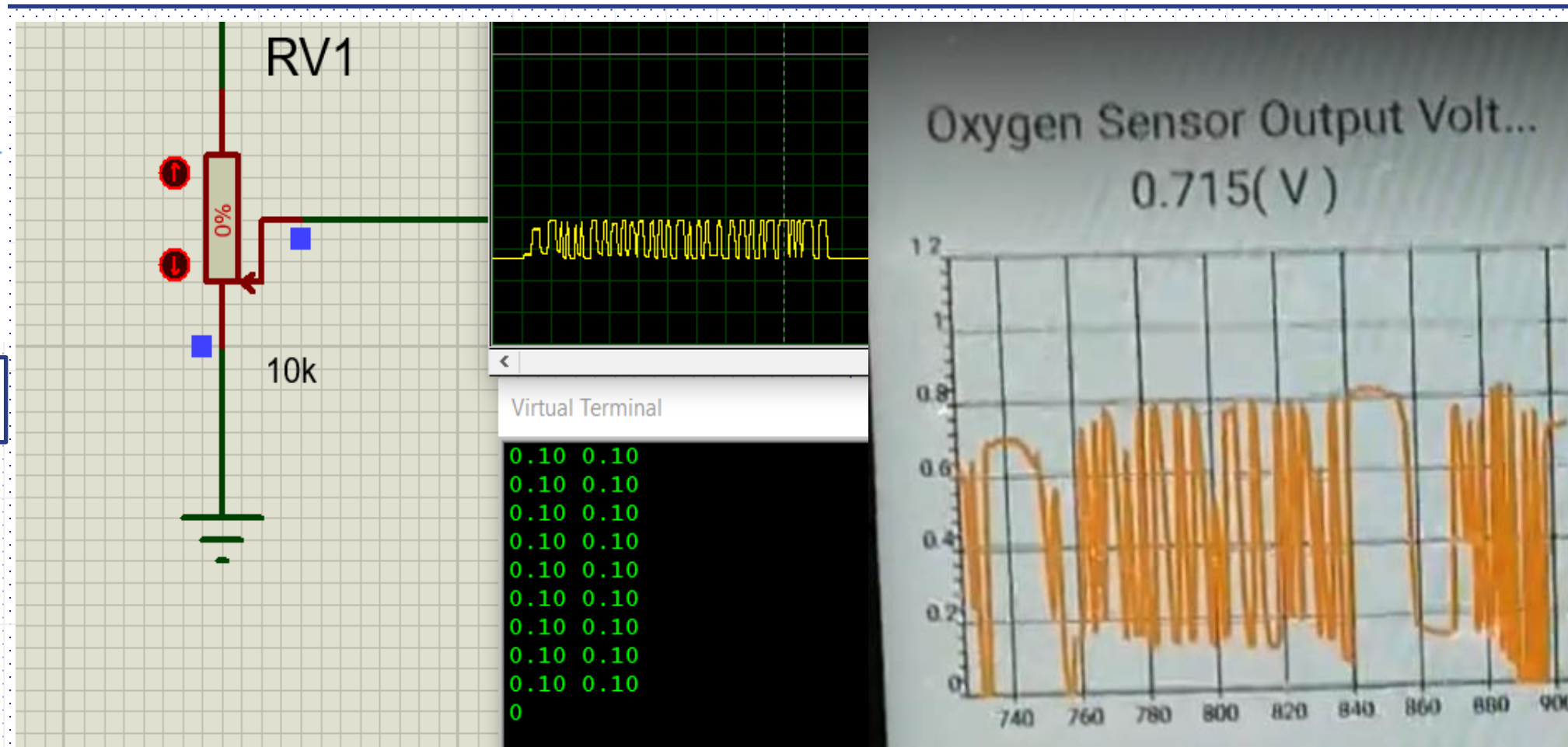


Figure 4.2: Oxygen signal in simulation of sensor1

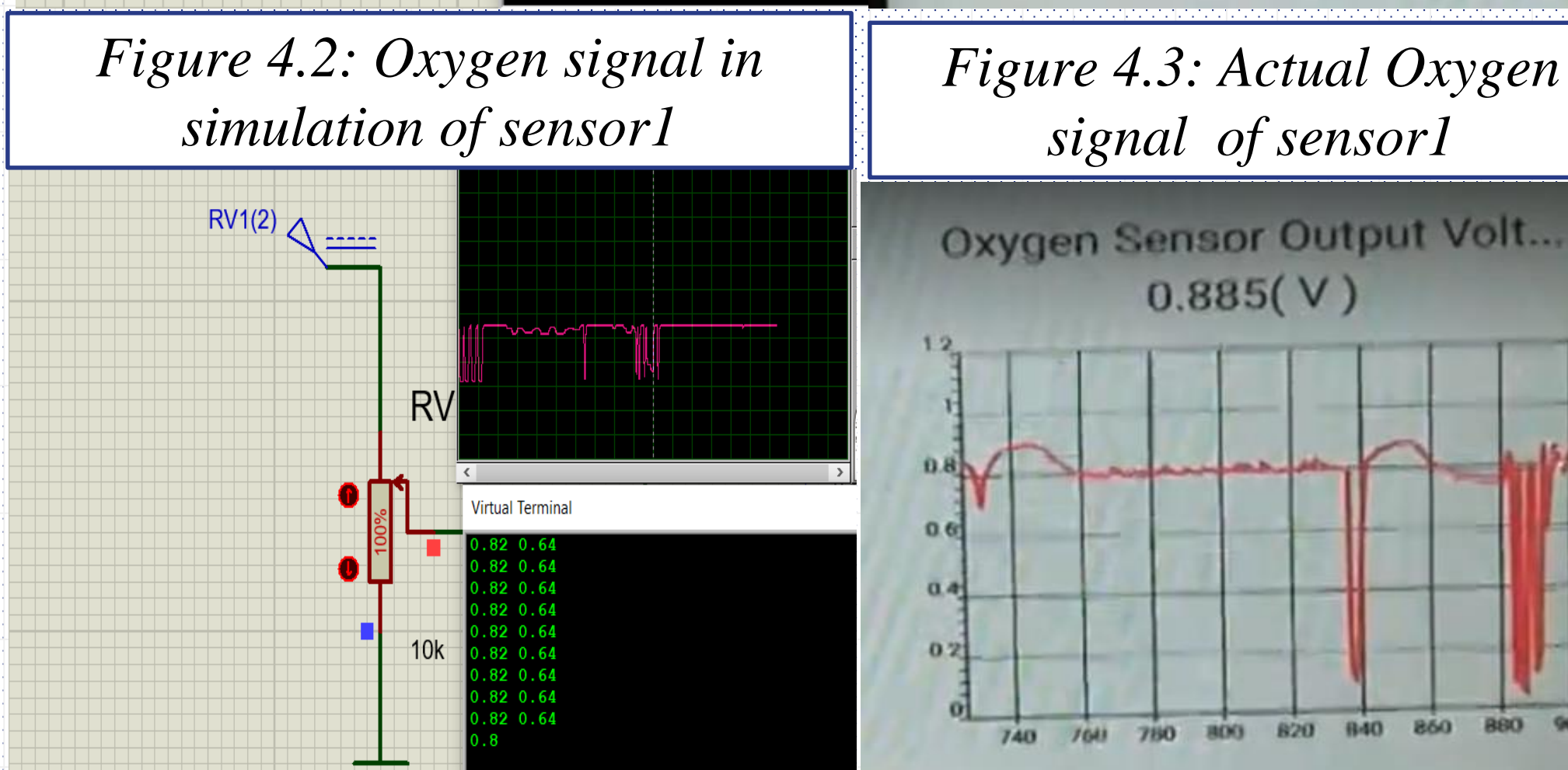


Figure 4.4: Oxygen signal in simulation of sensor2

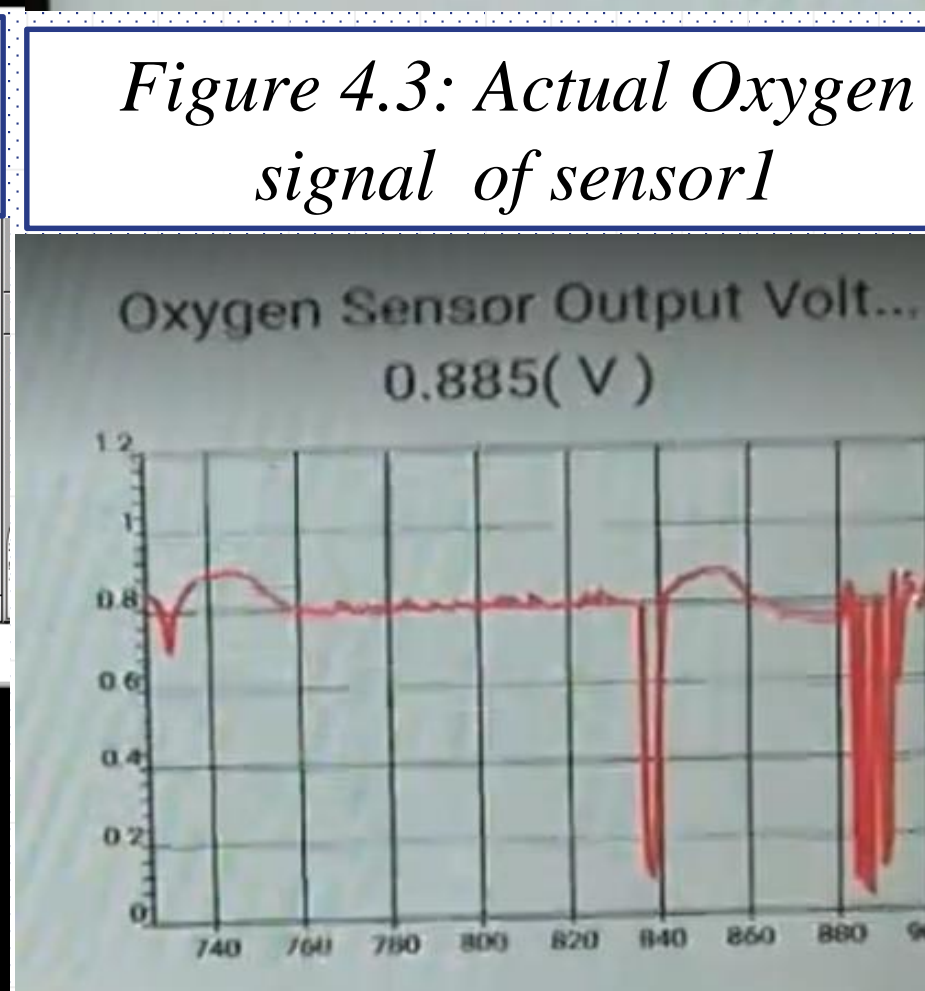


Figure 4.5: Actual Oxygen signal of sensor2

1. Simulation:

The simulation will depend on the electrical scheme to check the result:

- 1) Create a input signal change continuously from 0-100% like the A/F ratio of 2 oxygen sensor 1 and 2 at pin A0 and A1
- 2) The two simulation signals OS1 and OS2 will display on screen through port A and C.
- 3) Pin RXD and TXD on Arduino are connected to pin TXD and RXD on Virtual Terminal to display voltage value of two signals OS1 and OS2.

2. Discussion:

Satisfied:

- ✓ Calculate the voltage value and display the PWM with low error.
- ✓ Simulating the signal as the actual oxygen sensor.

Unsatisfied:

- ✓ The shape of pulse is still not smooth.
- ✓ Potentiometer can't give signal like oxygen voltage so the pulse signal cannot as exact as reality.